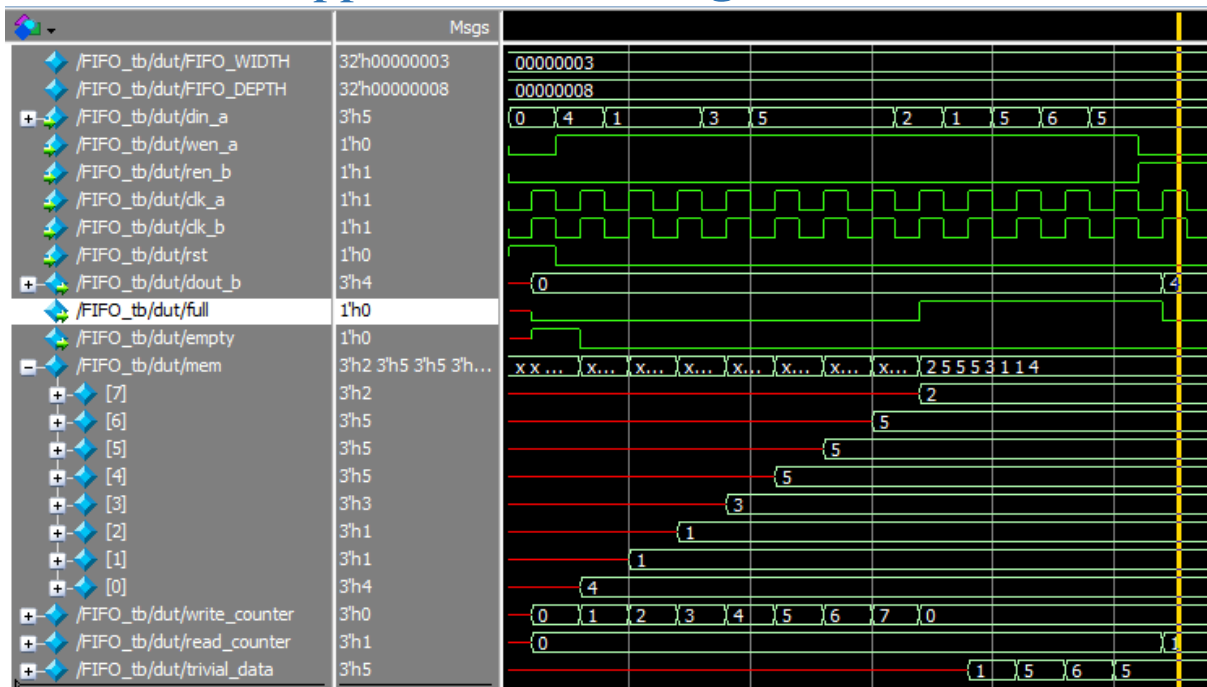


By

Mohamed Ahmed Mohamed
Hussein

FIFO Documentation


Test bench snippets(case: writing until full):



Notes:

- output
- Inputs
- you can copy the code
- focus on the full flag and the freezing of write_counter
- you can check the ignored data in trivial_data

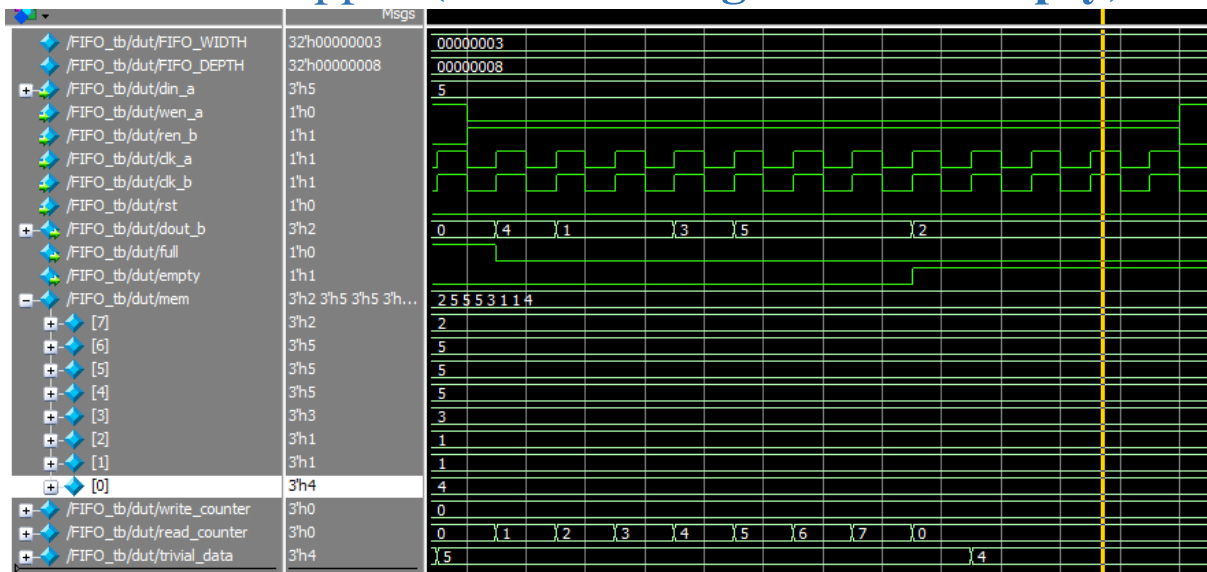
Test bench snippets(case: reading until it's empty):



Notes:

- output
- Inputs
- you can copy the code
- focus on the empty flag and the freezing of read_counter
- focus on dout_b you will find the data which was kept in the memory from previous writing

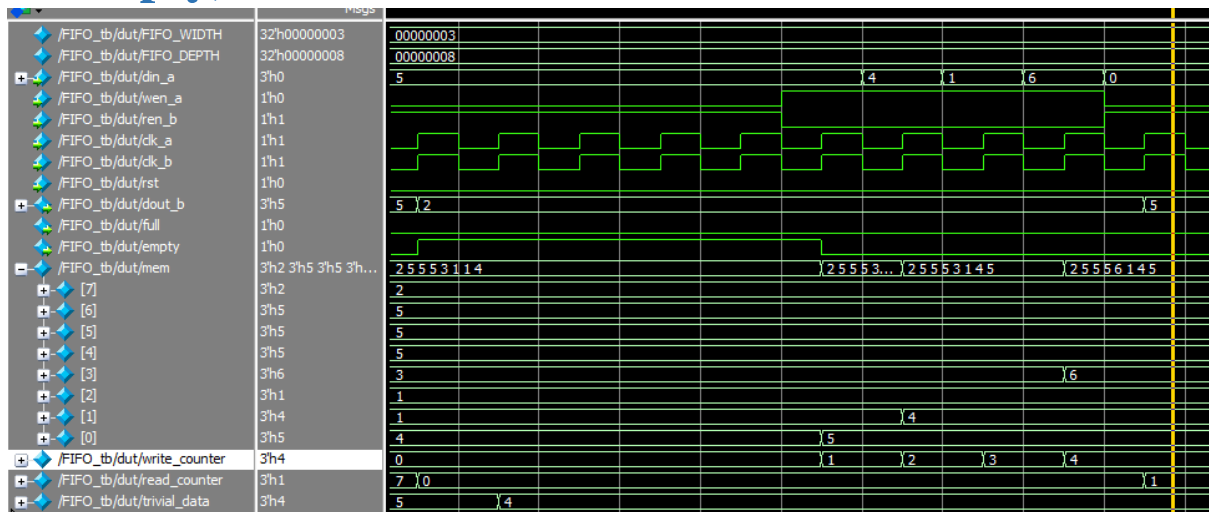
Test bench snippets(case: writing again so it's not full or empty):



Notes:

- output
- Inputs
- you can copy the code
- focus on the full and empty flags they are not asserted

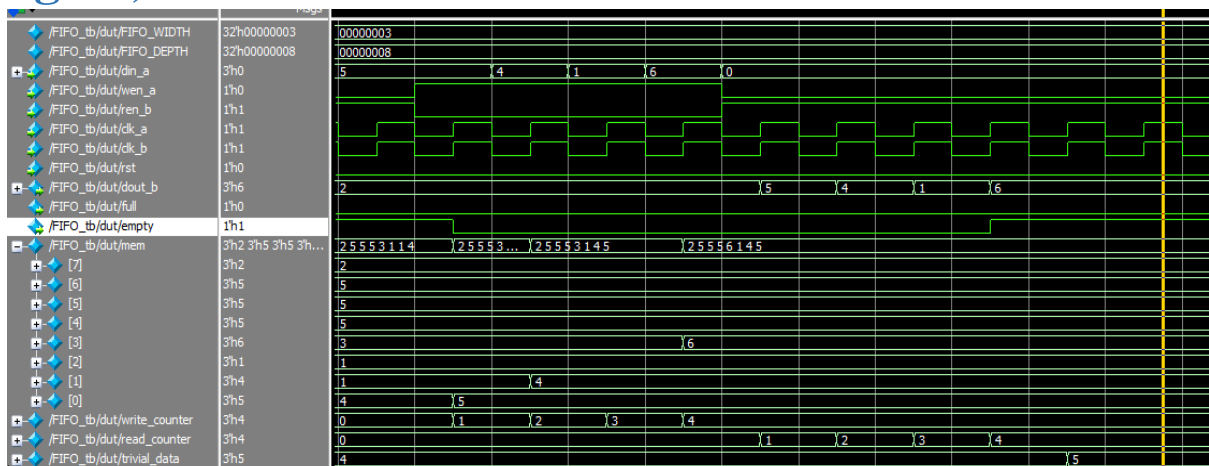Test bench snippets(case: reading until it's empty again):




Notes:


- output
- Inputs
- you can copy the code

- I made this case to test the functionality in the middle of the memory
- focus on the empty flag

Elaboration:

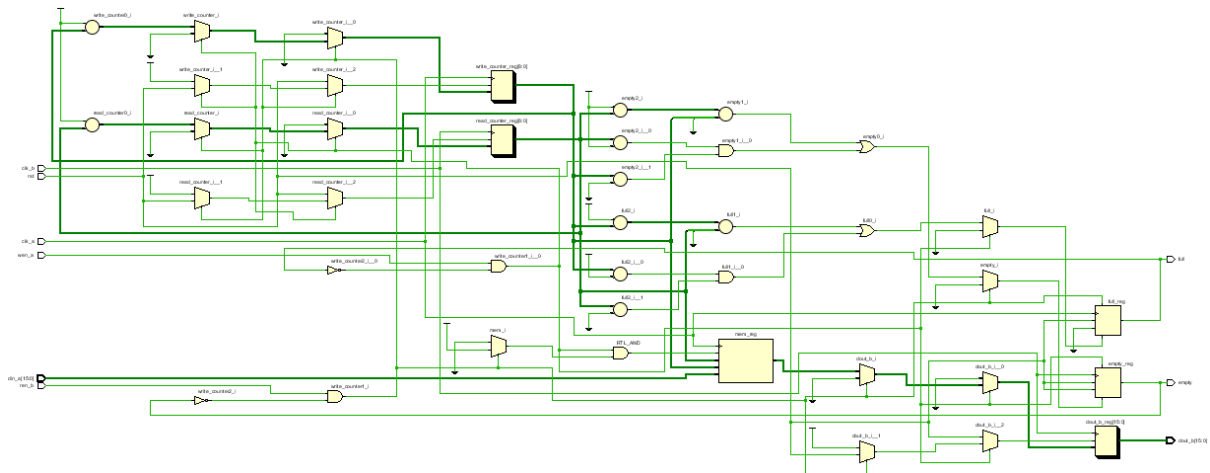

Synthesis:

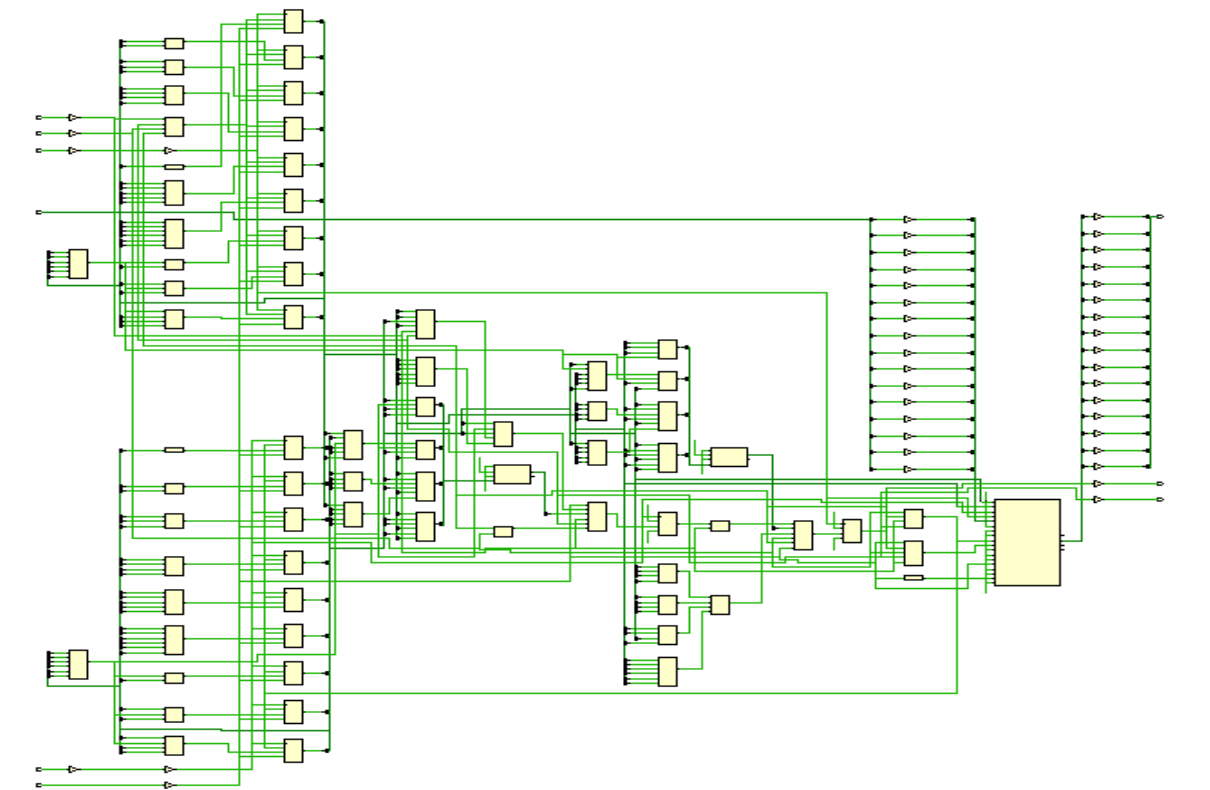

Utilization Report:

Name	Slice LUTs (20800)	Slice Registers (41600)	Block RAM Tile (50)	Bonded IOB (106)	BUFGCTRL (32)
FIFO_Model	39	20	0.5	39	2

Timing Report:

Tcl Console
Messages
Log
Reports
Design Runs
Timing
Utilization
Debug

Design Timing Summary

General Information
Timer Settings
Design Timing Summary
Check Timing (154)
Intra-Clock Paths
Inter-Clock Paths
Other Path Groups
User-Defined Paths

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): inf	Worst Hold Slack (WHS): inf	Worst Pulse Width Slack (WPWS): NA
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): NA
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: NA
Total Number of Endpoints: 113	Total Number of Endpoints: 113	Total Number of Endpoints: NA

There are no user specified timing constraints.

Implementation:

